

# Basic elements in sequential logic

Computer Fundamentals

Escuela Politécnica Superior U.A.M

# Summary of the lecture

## U3. Basic elements in sequential logic.

U3.1. Sequential Circuits.

U3.2. Latch. Types of latches.

U3.3. Flip-Flop. Types of Flip-Flops.

U3.4. Circuits with Flip-Flops.

Timing diagrams.


U3.5. Registers. Shift registers.

# Sequential Circuits

## Motivation:

There are problems that can not be solved following a combinational approach

 Example: Build a circuit to count the transitions of an input signal (CLK).




S<sub>1</sub> and S<sub>0</sub> functions can not be implemented using an standard combinational approach the same output is reached for the same input.

## Solution:

We need a new type of circuit in which the “next” output is a function of the inputs and the “previous” output value.

# Sequential Circuits

## COMBINATIONAL

 

CLK	S <sub>1</sub>	S <sub>0</sub>
0	0	0
1	0	1
2	0	0
3	0	1

**Let's take  
into account  
the previous  
input value**


## SEQUENTIAL

S <sub>1</sub>	S <sub>0</sub>	CLK	S' <sub>1</sub> S' <sub>0</sub>
0	0	↓	0 1
0	1	↓	1 0
1	0	↓	1 1
1	1	↓	0 0


## How to?:

- We need memory
- We need feedback (output signal is also an input) ... but how can we create and stable system

**Unstable  
feedback logic  
element**

 

**Stable feedback  
logic element**

 


**Stores (in memory)  
a '0' or a '1'**

# Sequential Circuits
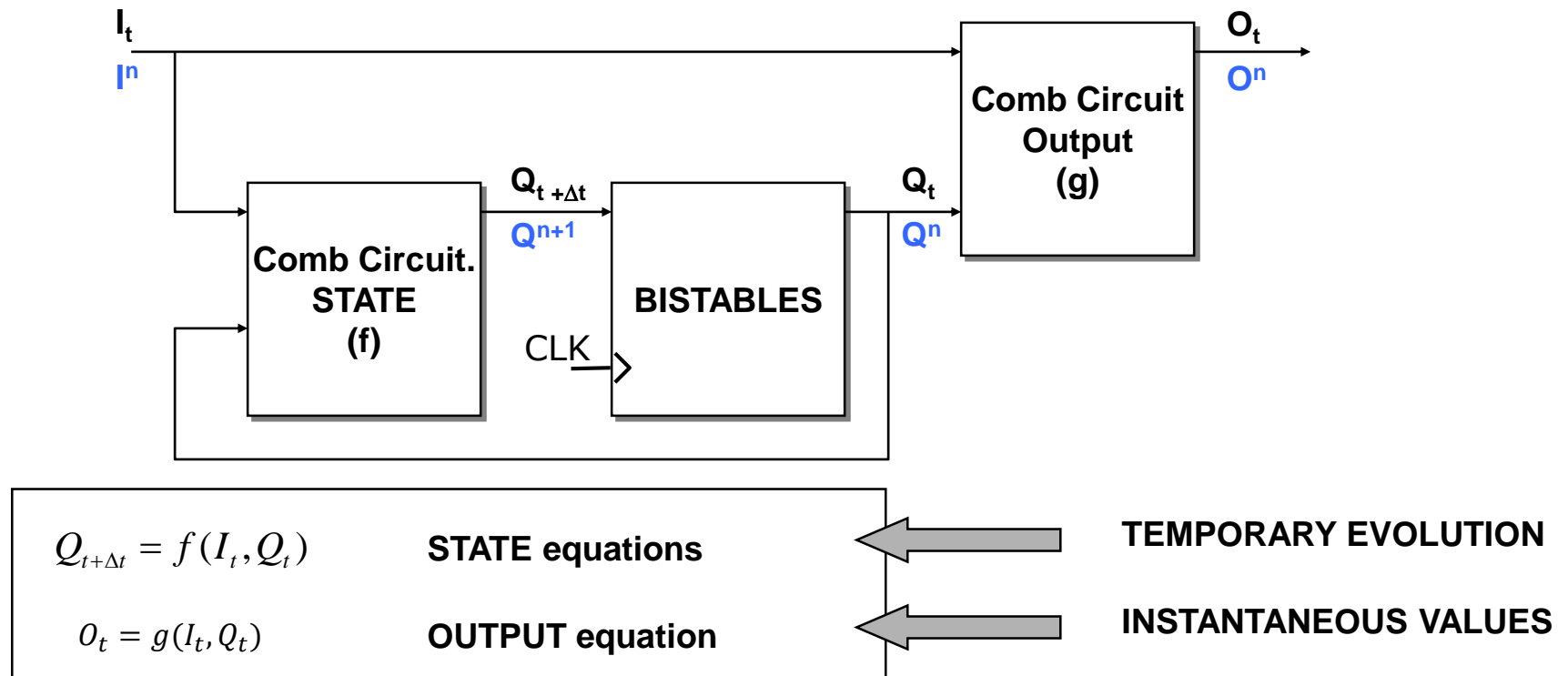
## Formal Definition

In a sequential circuit the outputs are dependent on the inputs and on the previous state.

- ✓ The value of the “previous” state is stored in elements with memory capacity.
- ✓ Each bit of information about the previous state is stored in a flip-flop.



# Asynchronous and Synchronous sequential logic

## ASYNCHRONOUS

The change of state and output is due to an input change

## SYNCHRONOUS

The change of state occurs when an event of a special signal (clock signal) gets into the flip-flops

### Classes

Level  
(latch)

High 

Low 

Edge  
(flip-flop)


Rise 

Drop 


There may be a change of state without changes at the input

Most common


# Flip Flop D

 

Timing diagram of a D type flip-flop

 


 Important timing parameters:  $t_{\text{setup}}$ ,  $t_{\text{hold}}$  y  $t_{\text{delay}}$



# Other Flip Flops

## Latch D

 


D	C	$Q^{n+1}$
X	0	$Q^n$
0	1	0
1	1	1

Closed  
Transparent  
mode


Synchronous  
by level

## Flip-Flop FF-T

 

T	CLK	$Q^{n+1}$
0	$\downarrow$	$Q^n$
1	$\downarrow$	$/Q^n$

## Flip-Flop FF-JK

 


J	K	CLK	$Q^{n+1}$
0	0	$\downarrow$	$Q^n$
0	1	$\downarrow$	0
1	0	$\downarrow$	1
1	1	$\downarrow$	$/Q^n$





# Conversion among Flip-Flops

 Example: from a flip-flop D, build a flip-flop T




T	$Q^n$	$Q^{n+1}$	D
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

  Example: from a flip-flop JK, build **a)** a flip-flop D y **b)** a flip-flop T



# Initialization of a Flip-Flop

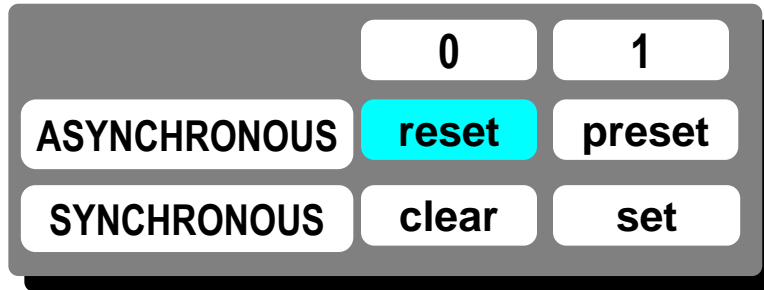


The initial value can be '0' or '1'

The asynchronous initialization is immediate

The synchronous initialization occurs in synchrony with the CLK


Initialization signals are generally active at low level

Example:  
Flip-Flop D with reset

 

The synchronous initialization can be considered as part of its functionalities


Example:  
Flip-Flop D with clear

 

# Application: Loading a Flip-Flop

In the synchronous Flip-Flops, it is possible to load a '0' or a '1' by means of a special input known as "L" (Load). Similar to *enable* in the combinational circuits.

 Example: from a flip-flop D, build a flip-flop T with Load Functionality




L	Dat	T	$Q^{n+1}$
1	0	X	0
1	1	X	1
0	X	0	$Q^n$
0	X	1	$/Q^n$

# Registers
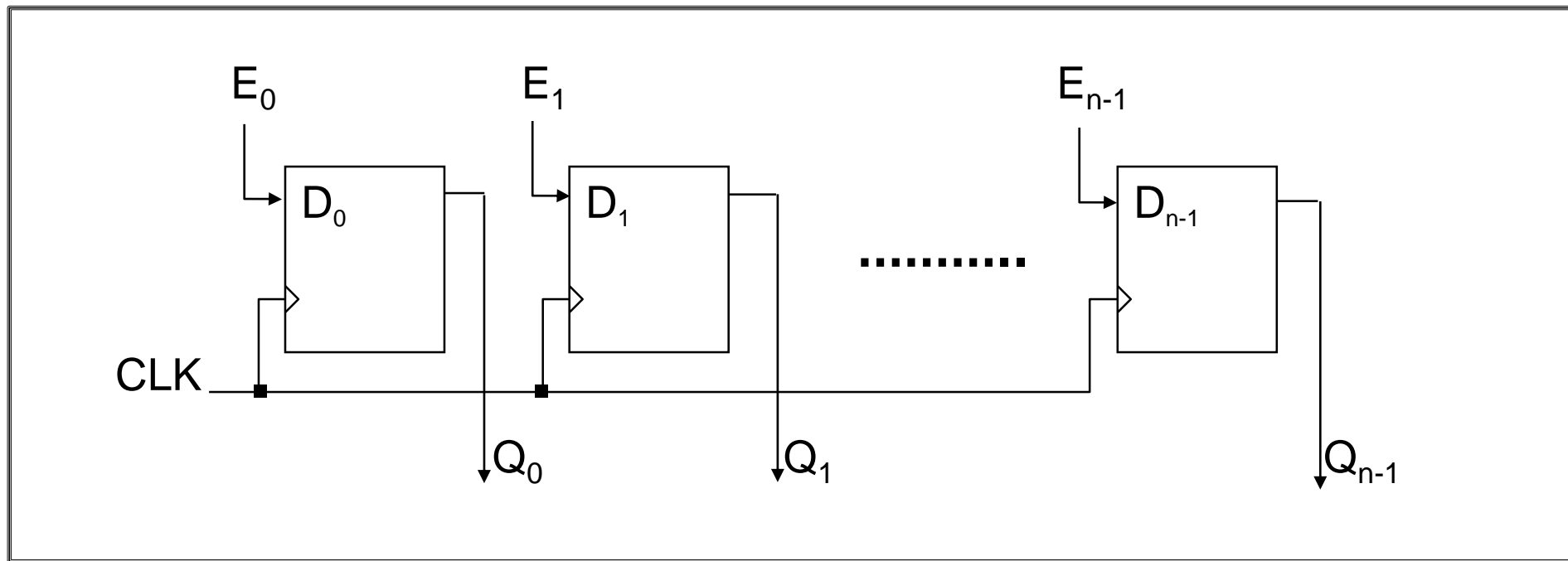
## Register:

- ✓ Sequential system formed by a set of flip-flops of the same type sharing a CLK signal.




**Example:** Register of n bits

# Registers
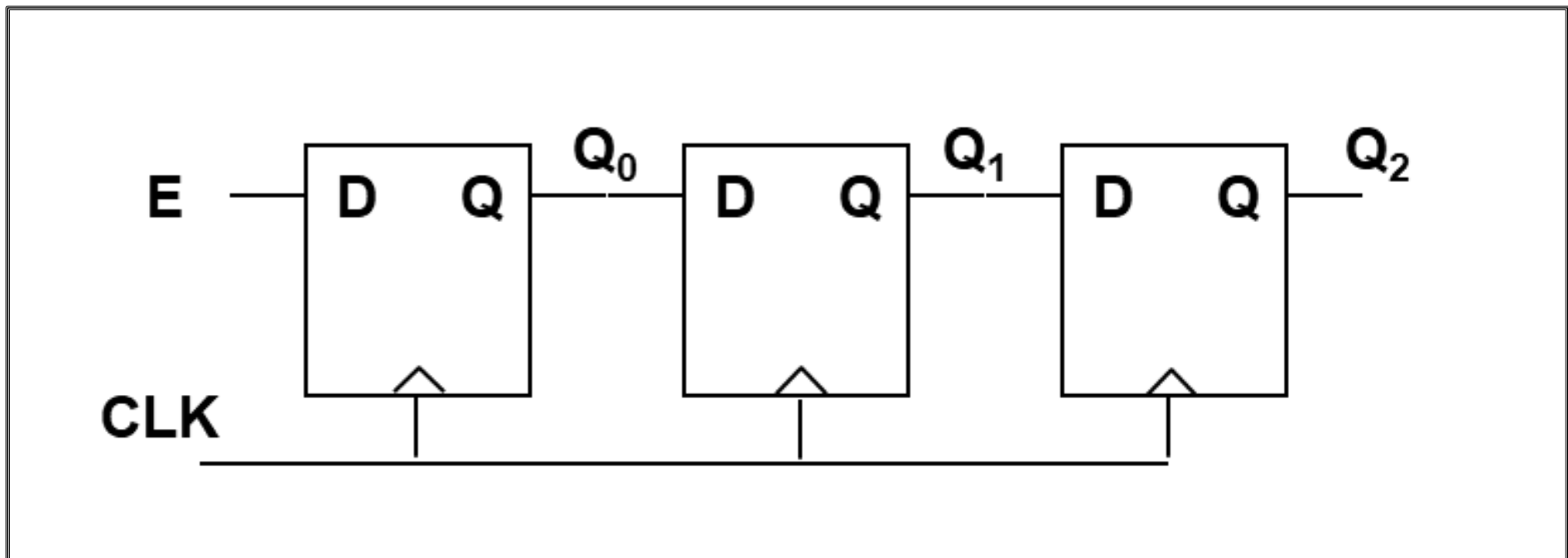
## Shift register:




- ✓ Output of the FF is connected to the input of the next FF



**Example:** Shift Register of 3 bits


# Timing diagrams with Flip-Flops

   Example: Complete the time diagram of the figure for each of these circuits


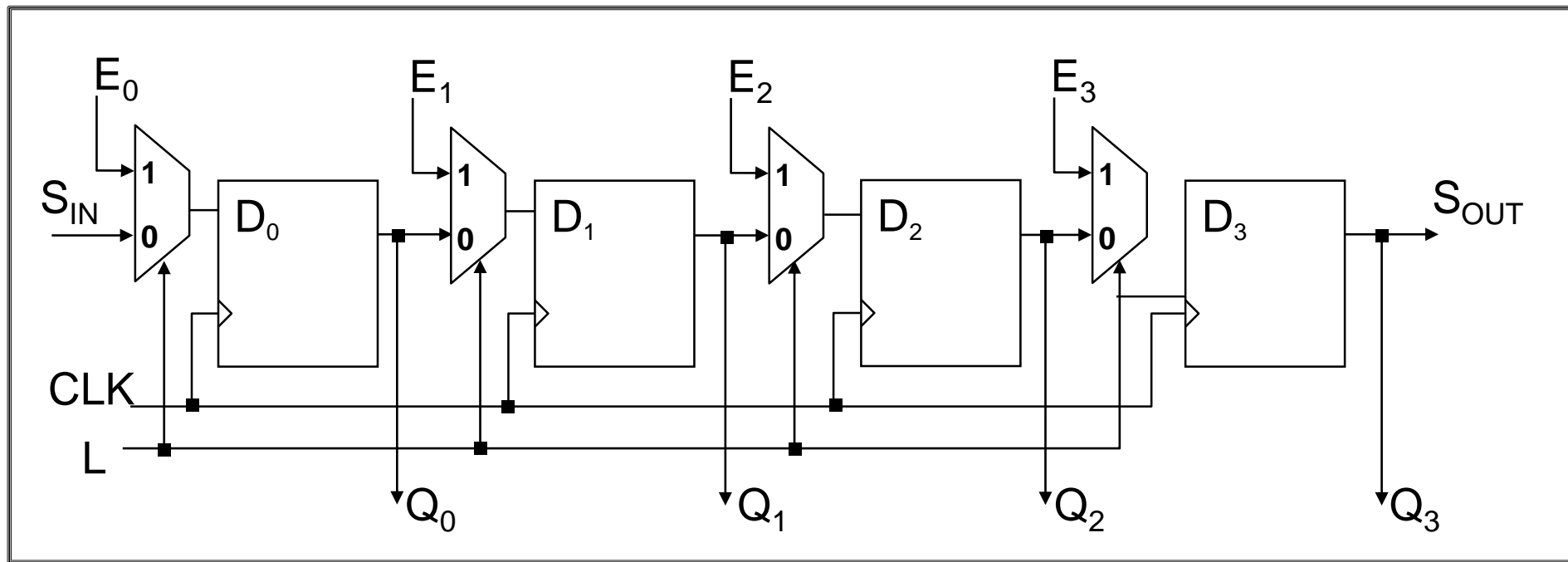
# Shift Register with Load input


- ✓ **Register with load input:** A load signal L, allows to load synchronously in the register any desired value.



**Example:** Shift register (4bits) with load input.

# ANNEX

## Asynchronous Flip-Flop RS

 








S	R	$Q_t$	$Q_{t+\Delta t}$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

a, b) Keep the state

c, d) Reset

e, f) Set

g) Priority registration

       




# ANNEX


## Asynchronous flip-flop RS

With  $R=S=1$ , outputs are not complementary and depend on the internal design of the flip-flop.


### Priority Registration

 

### Priority Erasure

 

 
**How to get that  $\overline{Q}$  is always  $\overline{Q}$ ?**



# ANNEX


## Synchronous Flip-Flop RS

### Active by level

 

### Active by edge (edge-triggered)

(NOT RECOMMENDED)

 

### Active by edge (master-slave)

