

Unit 1: Digital design and VHDL

Escuela Politécnica Superior - UAM

Outline

- **Introduction**
- Combinational logic
- Combinational circuits
- Sequential logic
- Structural modeling
- *Testbenches*

Introduction

- *Hardware description language* (HDL) allows for designing the functionality of a digital circuit without writing logic functions nor gates. Several software tools produce and **synthesize** the circuit that implements that functionality.
- Commercial circuits are designed with HDL languages.
- The two main HDL languages are:
 - **VHDL**
 - Designed in 1981 by the U.S Department of Defense.
 - It was defined as a standard IEEE-1076 in 1987
 - **Verilog**
 - Design in 1984 by Gateway Design Automation.
 - It was defined as a standard IEEE-1364 in 1995

Simulation and synthesis

- **Design and synthesis**

- Behavioral description of the digital system, sometimes with internal components and their connections
- It translates the HDL code in a circuit (*netlist*) which describes the hardware (a gate list and interconnecting nets)

- **Simulation**


- Some values are driven as inputs
- The outputs are checked
- Much time/money is saved by debugging the circuit with simulations instead of using real hardware

IMPORTANT:

- ✓ Not every design which can be simulated is also synthesizable.
- ✓ When describing HDL circuits, it is important to think which is the **hardware** that should be implemented (**different than programming software**).

Entity - Architecture

 
- The entity is used to describe the circuit like a black-box. It only describes its interface (the input and output **ports**)



Equivalent to C

```
float Average(float a, float b) {  
    float c;  
    c = (a+b) / 2;  
    return c;  
}
```

 
- The circuit content is modeled inside the architecture



```
float Average(float a, float b) {  
    float c;  
    c = (a+b) / 2;  
    return c;  
}
```

- An entity may have several architectures

PORTS: The interface

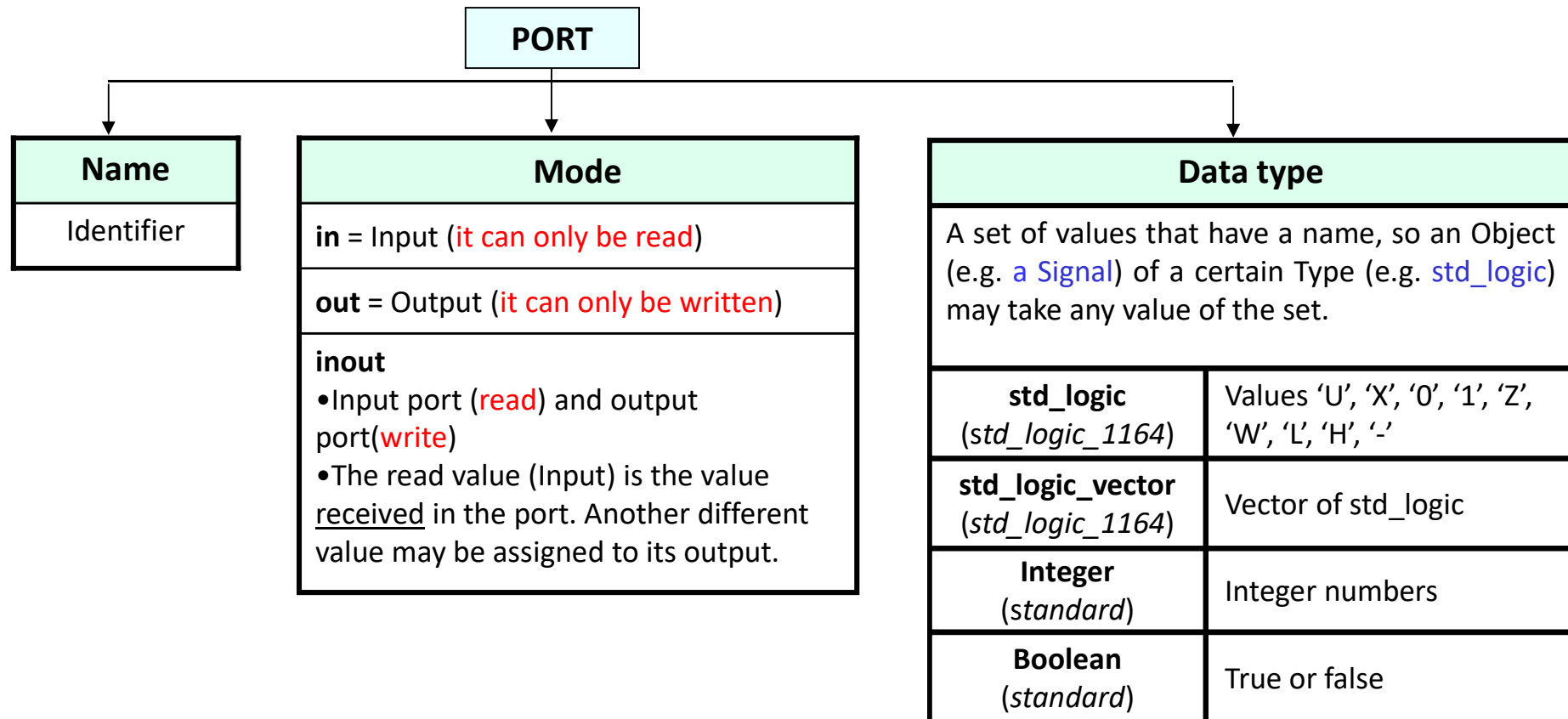


VHDL code example

```
LIBRARIES { library IEEE;                                -- similar to .h define
           { use IEEE.std_logic_1164.all;                -- To use std_logic

ENTITY { entity inverter is
      {   port (a : in std_logic;
          {       y : out std_logic);
      { end inverter;

 ARCHITECTURE { architecture behavioral of inverter is
            { begin
            {     y <= not a;                                -- assignment with arrow
            { end behavioral;
```



Synthesis of VHDL code

VHDL:


```
architecture behavioral of example is
```

```
begin
```

```
    y <= (not a and not b and not c) or (a and not b and not c) or  
        (a and not b and c);
```

```
end behavioral;
```

Synthesis:

 

VHDL syntax

- It does not distinguish upper from lower case (*case insensitive*)
 - Example: `reset` and `Reset` are the same signal.
 - Recommendation: Write the same upper and lower-case letters to facilitate the reading and searching.
- The names cannot start with numbers
 - example: `2mux` is not a right name.
- Spaces, tabs and carriage returns are ignored
- Comments:
 - From a double-hyphen until the end of the line.
 - `/* Block comment */`

VHDL syntax: Identifiers

IDENTIFIER

Names and labels that are used to identify: Constants, Signals, Processes, Entities, etc.

Length (Number of label characters): Without restrictions

Reserved word in VHDL cannot be identifiers

In VHDL, an identifier in upper-case is the same as in lower-case

They are composed by numbers, letters (upper or lower-case) and underscore “_” with the following rules.



Rules to specify an identifier	<i>wrong</i>	<i>right</i>
The first character must be always an upper or lower-case letter	4Add	Add4
The second character cannot be an underscore (_)	S_4bits	S4_bits
Two consecutive underscores are not allowed	Sub__4	Sub_4_
An identifier cannot use special symbols	Clear#8	Clear_8

Outline

- Introduction
- **Combinational logic**
- Combinational circuits
- Sequential logic
- Structural modeling
- *Testbenches*

std_logic type

- The values '0' and '1' of bit-type cannot model every state that a real digital signal can take.
- IEEE.std_logic_1164 package defines **std_logic type**, which defines every possible state:

- U Not initialized, default value
- X Unknown, multisource line (short circuit)
- 0 Logic 0
- 1 Logic 1
- Z High impedance (tri state)
- W Weak unknown, bus termination
- L Weak 0, pull-down resistor
- H Weak 1, pull-up resistor
- Don't care, used as a wildcard in synthesis

std_logic_vector type defines a *bit array* of **std_logic**.

Unsigned and signed types

- IEEE.numeric_std package define **unsigned** and **signed** types for representing unsigned and signed numbers. These types must be used for arithmetic operations. These types are vectors of **std_logic** equivalent to std_logic_vector but offering the following operations:
- Sign change operations: “-” and “*abs*”
- Arithmetic operations: “+”, “-” and “*” (multiply)
- Comparison operations: “>”, “<”, “<=”, “>=”, “=” and “/=” (different)
- Logic shifts: “*sll*” (left) y “*srl*” (right)
- Arithmetic shifts: “*sla*” (left) y “*sra*” (right)
- Rotations: “*rol*” (left) y “*ror*” (right)
- Change size (number of bits): “*resize*”

Bitwise operators


```
entity gates is
port (a, b: in std_logic_vector(3 downto 0);
      y1, y2, y3, y4, y5: out std_logic_vector(3 downto 0));
end gates;
```

```
architecture behav of gates is
begin
```

```
-- They are automatically adapted
-- to one bit or a bus
```

```
y1 <= a and b; -- AND
y2 <= a or b; -- OR
y3 <= a xor b; -- XOR
y4 <= a nand b; -- NAND
y5 <= a nor b; -- NOR
```


```
end behav;
```

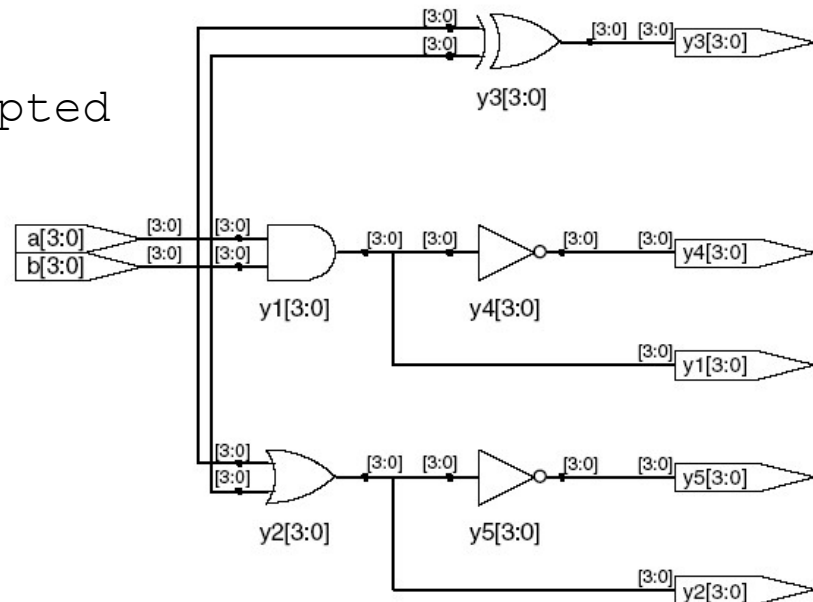

Conditional assignment: when ... else

```
entity mux2a1_4bits is
port(d0,d1 : in std_logic_vector(3 downto 0);
      s : in std_logic;
      y : out std_logic_vector(3 downto 0));
end mux2a1_4bits;
```
 
```
architecture behav of mux2a1_4bits is
begin
    y <= d0 when s = '0' else d1;
end behav;
```



Conditional assignment: with ... select

```
entity deco2a4 is
port(a : in std_logic_vector(1 downto 0);
      y : out std_logic_vector(3 downto 0));
end deco2a4;

architecture behav of deco2a4 is
begin

    with a select
        y <= "0001" when "00",
              "0010" when "01",
              "0100" when "10",
              "1000" when others;    -- last case, it should
                                   -- be included

end behav;
```


Internal signals

architecture behav of fulladder is

```
signal p, g : std_logic; -- Internal signal declaration
                           -- goes between architecture and begin
```

begin


```
p <= a xor b;
```

```
g <= a and b;
```

```
s <= p xor cin;
```

```
cout <= g or (p and cin);
```

end behav;

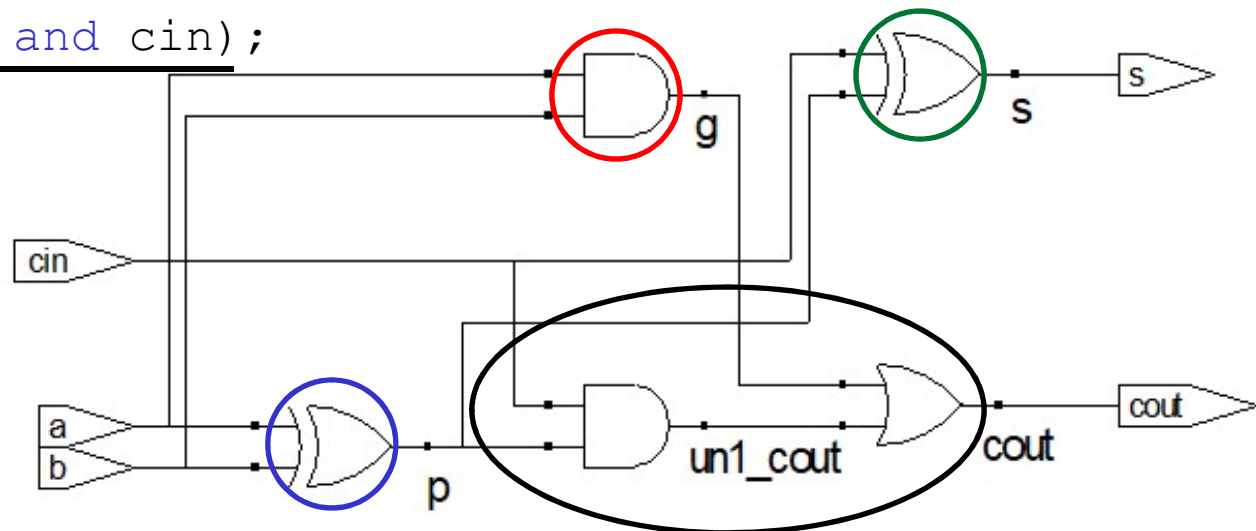

Concurrency

```
architecture behav of fulladder is
    signal p, g : std_logic;
begin
    p <= a xor b;           -- The line order is not
    g <= a and b;           -- important, all the hardware
    s <= p xor cin;         -- is executed simultaneously
    cout <= g or (p and cin);
end behav;
```

```
-----
architecture behav of fulladder is
    signal p, g : std_logic;
begin
    cout <= g or (p and cin); -- This is the same circuit
    s <= p xor cin;           -- P is assigned in the third
    p <= a xor b;             -- line but hardware
    g <= a and b;             -- is concurrent
end behav;
```

Operator precedence

- Order in which the operators in an expression are evaluated without parentheses
- Recommendation: use parentheses

First

Operator	Operation
not	NOT
* / %	mult div module
+ -	add subtract
< <= > >=	compare
= /=	equal different
and nand	AND NAND
xor xnor	XOR XNOR
or nor	OR NOR

Last

Number formats and bits

Format	Number of bits	Base	Memory
<code>'1'</code>	1	Binary	1
<code>"101"</code>	>1	Binary	101
<code>X"AF"</code>	>1	Hexadecimal	10101111
1	It depends	Decimal	0...00001
-2	It depends	Decimal	1...11110 (C2)
1.5	It depends	Decimal	IEEE-754

The signal values are assigned with a left arrow:

```
a_bit <= '1';
```

```
a_bus <= "101";
```

```
a_int <= 1;
```

Bit manipulation

```
signal a : std_logic_vector(3 downto 0);  
signal b : std_logic_vector(0 to 3);  
...  
a <= "0101";  
b <= "0101";
```

-- it is equivalent to:

```
a(3) <= '0';   a(2) <= '1';   a(1) <= '0';   a(0) <= '1';  
b(3) <= '1';   b(2) <= '0';   b(1) <= '1';   b(0) <= '0';
```

a	Position	3	2	1	0
	Value	0	1	0	1
b	Position	0	1	2	3
	Value	0	1	0	1


Bit manipulation

```
signal y : std_logic_vector(7 downto 0);  
signal a, b : std_logic_vector(3 downto 0);  
...  
-- the & operator in VHDL means concatenate  
y <= a & b(3) & '0' & b(2 downto 1);
```

-- it is equivalent to:


```
y(7) <= a(3); y(6) <= a(2); y(5) <= a(1); y(4) <= a(0);
```
 
```
y(3) <= b(3); y(2) <= '0'; y(1) <= b(2); y(0) <= b(1);
```



Bit manipulation
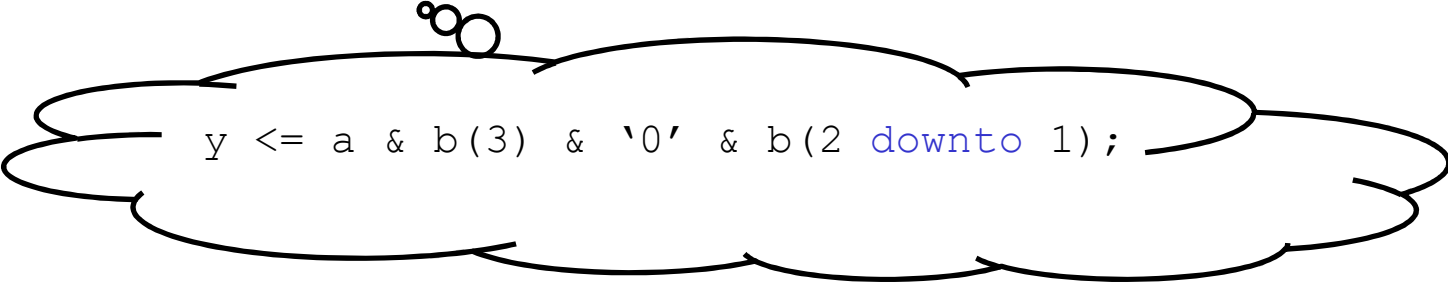
```
signal y : std_logic_vector(7 downto 0);  
signal a, b : std_logic_vector(3 downto 0);  
...  
-- Any partial manipulation can be done while the  
-- destination and source lengths match.  
y(7 downto 4) <= a;  
y(3) <= b(3);  
y(2) <= '0';  
y(1 downto 0) <= b(2 downto 1);  
  
-- the signal "y" gets the same value as in the  
-- previous slide
```



```
y <= a & b(3) & '0' & b(2 downto 1);
```

Bit manipulation

```
signal y : std_logic_vector(7 downto 0);
signal a, b : std_logic_vector(3 downto 0);
...
-- in VHDL it is allowed to make index-based assignments
-- apart from order-based assignments (left to right).
-- (aggregates)
y <= (3 downto 2 => a(2), 4 => b(1), 5 => '1',
      others => '0');      -- others means "the rest of bits"

-- it is equivalent to:
y(7) <= '0'; y(6) <= '0'; y(5) <= '1'; y(4) <= b(1);
y(3) <= a(2); y(2) <= a(2); y(1) <= '0'; y(0) <= '0';


-- common in bus initialization:
y <= (others => '0'); -- all the bits get '0' value
```


Z: high impedance

VHDL:

```
signal y, a: std_logic_vector(3 downto 0);  
signal en : std_logic;  
...  
y <= (others => 'Z') when en = '0' else a;
```

Synthesis:

 

Outline

- Introduction
- Combinational logic
- **Combinational circuits**
- Sequential logic
- Structural modeling
- *Testbenches*

Combinational circuits

- Most of combinational circuits can be defined with concurrent assignments (previously seen)
- There is also sequential code (it is executed line by line, like in software, without concurrence, so **the order of the code is important**) but is encapsulated in `processes` (apart from functions and procedures which are not explained in this course)
- Inside the processes (and only inside of them) you can use `if`, `case`, `for` and `while`

Process

“Process” structure:

```
architecture ArchName of EntityName is
    -- declarative part, internal signals of the architecture
begin
    -- The processes must be implemented between the “begin” and
    -- “end” of the architecture
    [LABEL:] process(sensitivity list) -- The label is optional
        -- Declarative part, variables but not signals, for
        -- internal use
    begin
        -- code;
    end process [LABEL];
end ArchName;
```

Every time one signal of the sensitivity list is changed, the **code** is executed. From VHDL-2008, the sensitivity list can be **all**, avoiding to choose specific signals.

if

```
if condition_1 then
  -- sec instr 1
[elsif condition_2 then
  -- sec instr 2]
[elsif condition_3 then
  -- sec instr 3]
[else
  -- instr by default]
end if;
```

Similar to *when...else*
conditional assignment

Example

```
CTRL: process(all) -- or (level)
begin
  if level > 60 then
    a <= "11";
  elsif level > 40 then
    a <= "10";
  elsif level > 20 then
    a <= "01";
  elsif level > 15 then
    a <= "00";
  end if;
end process CTRL;
```

Attention: In combinational logic, the “else”
branch must be present

case

```
case expression is
  when case_1 =>
    -- instr 1
  when case_2 =>
    -- instr 2
  when others =>
    -- by default
end case;
```

Similar to *with...select*
conditional assignment

Example

```
MUX: process(all)
    -- or (sel, a, b, c, d)
begin
    case sel is
        when "11" => y <= d;
        when "10" => y <= c;
        when "01" => y <= b;
        when others => y <= a;
    end case;
end process MUX;
```

Attention: In combinational logic, the “when others”
branch must be present

for

```
[LABEL:] for index in range loop
    -- sec instr
end loop [LABEL];
```

Example

```
AND8: process (all)
begin
    for i in 0 to 7 loop
        y(i) <= a(i) and b(i);
    end loop;
end process AND8;
```

```
AND8: process (all)
begin
    for i in 7 downto 0 loop
        y(i) <= a(i) and b(i);
    end loop;
end process AND8;
```

```
y <= a and b;    -- This solution is easier
                  -- because and is a bitwise operator
                  -- Besides, a process is not mandatory
```

while

```
[LABEL:] while condition loop
    -- sec instr
end loop [LABEL];
```

Example

```
process (...)
begin
    while a = '1' loop
        ...
        ...
        ...
    end loop;
end process;
```


When/else and with/select inside a process

```
process(all)
begin
    y <= a and b when sel = '0' else c;
    ...
end process;
```

```
process(all)
begin
    with sel select
    y <= "0001" when "00",
        "0010" when "01",
        "0100" when "10",
        "1000" when others;
    ...
end process;
```

Concurrent or sequential?

- Hardware is concurrent. What's the point of writing a sequential code?

```
...  
a <= '0';  
...  
a <= '1';  
...
```

a=? a=X

```
process(all)  
begin  
    ...  
    a <= '0';  
    ...  
    a <= '1';  
end process;
```

a=? a='1'

Signal update inside processes

- The time is “**paused**” when a process is executed. The signals that are written receive the new value after finishing the process or after a wait.

```
process(all)
begin
    ...
    a <= '0';
    b <= not a;
    ...
end process;
```

Signal	Before the process	After the process
a	'1'	'0'
b	?	'0'

Signal update inside processes


- The time is “**paused**” when a process is executed. The signals that are written receive the new value after finishing the process or after a wait.

```

Process                                -- without sensitivity list
begin
    while simulating = '1' loop
        clk <= '0';      ← '?'
        wait for 10 ns;   ← '0'
        clk <= '1';      ← '0'
        wait for 10 ns;
    end loop;
    wait ;                ← '1'
    -- it prevents the continuous execution of the
    -- while structure when simulating = '0'
end process;
    
```

Signal	Before the process	Before 1 st wait	After 1 st wait	Before 2 nd wait	After 2 nd wait
clk	?	?	'0'	'0'	'1'

 Time “**does continue**” during the execution of a *wait*



**Attention: The *wait* sentence cannot be used for real hardware.
It can only be simulated.**

Conditional assignments and loops: Summary

- Inside and outside processes
 - ✓ When – elseelse – ;
 - ✓ With – selectwhen others ;

- Inside processes
 - ✓ If ** then – ; elsif – ; else – ; end if ;
 - ✓ Case ** is when – ;when others – ; end case;
 - ✓ For ** in ** downto/to ** loop – ; end loop ;
 - ✓ While ** loop – ; end loop;

Combinational logic: Inside or outside the process?

- Except in the use of loops, any combinational code written in a process can be written outside the process (concurrent sentences) and vice versa.
- If a process is used, longer code required but more flexibility (using if / case, overwriting signals, etc).

Outline

- Introduction
- Combinational logic
- Combinational circuits
- **Sequential logic**
- Structural modeling
- *Testbenches*

Sequential logic


- In VHDL, flip-flops (or registered signals) are described using always this template:
 - **Using a process**
- Other descriptions may reach equivalent simulations, but they do not synthesize the same hardware

D-type Flip-Flop

```
entity flop is
port(Clk : in std_logic;
      D : in std_logic_vector(3 downto 0);
      Q : out std_logic_vector(3 downto 0));
end flop;
```

```
architecture synthesizable of flop is
begin
```

 
```
REG: process(all)
begin
    if Clk = '1' and Clk'event then --if rising_edge(Clk) then
        Q <= D;
    end if;
end process;
end synthesizable;
```



D-type Flip-Flop with asynchronous Reset


-- Reset is added in the entity
 
```
architecture synthesizable of flop is
begin
    process(all)
    begin
        if Reset = '1' then
            Q <= (others => '0');
        elsif Clk = '1' and Clk'event then
            Q <= D;
        end if;
    end process;
end synthesizable;
```



D-type Flip-Flop with synchronous Reset

 
```
architecture synthesizable of flop is
begin
  process(all)
  begin
    if Clk = '1' and Clk'event then
      if Reset = '1' then
        Q <= (others => '0');
      else
        Q <= D;
      end if;
    end if;
  end process;
end synthesizable;
```



D-type Flip-Flop with Enable

-- *En* is added in the entity

 
```
architecture synthesizable of flop is
begin
  process(all)
  begin
    if Reset = '1' then
      Q <= (others => '0');
    elsif Clk = '1' and Clk'event then
      if En = '1' then
        Q <= D;
      end if;
    end if;
  end process;
end synthesizable;
```



 1.11, 1.14

Latch

```
architecture synthesizable of latch is
begin
  process(all)
  begin
    if CE = '1' then -- without edge, only by level
      Q <= D;
    end if;
  end process;
end synthesizable;
```



Unwanted latches

```
process(all)
begin
    if a = "00" then
        b <= "11";
    elsif a = "01" then
        b <= "10";
    elsif a = "10" then
        b <= "00";
    end if;
end process;
```

Which is the value of *b* when *a*="11"?

b keeps the previous value => Latch


Attention: unwanted latches are synthesized when the destination value does not receive values in every path. In this course the latches are not used, but a code can generate them unintentionally. If the synthesized hardware includes latches, it will be considered as an error, especially if the code should be combinational.

Outline

- Introduction
- Combinational logic
- Combinational circuits
- Sequential logic
- **Structural modeling**
- *Testbenches*

Structural model

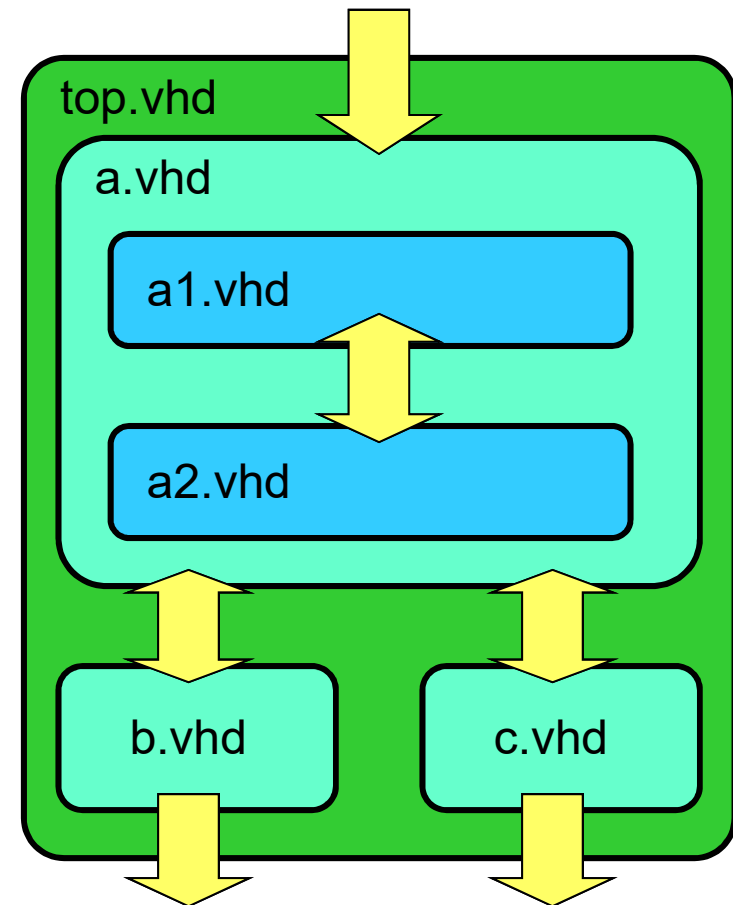- The basic components are used as elements of other bigger elements.
- They are essential for code reuse.
- It allows the designer to mix components design with different methods:
 - Schematics
 - VHDL, Verilog
- It generates more legible and portable designs.
- It is necessary for *top-bottom* or *bottom-up* designs.



How to instantiate a component

```
entity top is  
port  
  ( ... );  
end top;
```

```
architecture hierarchical of top is  
  signal s1, s2 : std_logic;
```

```
    component a  
    port  
      (entrada: in std_logic;  
        salida: out std_logic);  
    end component;
```

```
begin
```

```
  u1: a  
    port map  
      (entrada => s1,  
        salida => s2);
```

```
end hierarchical;
```

Example of hierarchical design: Internal component

```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;
```

```
ENTITY myand2 IS PORT (  
    x, y: IN std_logic;  
    z: OUT std_logic);  
END myand2;
```

```
ARCHITECTURE archand2 OF myand2 IS  
BEGIN  
    z <= x AND y;  
END archand2;
```

Internal component description:
“2-input AND gate”



Example of hierarchical design: top-level component

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY myand4 IS PORT (
    a, b, c, d: IN std_logic;
    z: OUT std_logic);
END myand4;
```

Top-level component:
“4-input AND gate”



```
ARCHITECTURE archmyand4 OF myand4 IS

COMPONENT myand2 PORT (
    x, y: IN std_logic;
    z: OUT std_logic);
END COMPONENT;
```

Component declaration




```
SIGNAL s1, s2: std_logic;
```

Component instantiation. Associated by name

```
BEGIN
    a1: myand2 PORT MAP (x=>a, y=>b, z=>s1);
    a2: myand2 PORT MAP (z=>s2, y=>c, x=>d); -- The order can be varied
    a3: myand2 PORT MAP (x=>s1, y=>s2, z=>z);

-- Apart from the instantiations, more code can be added in the architecture
END archmyand4;
```



Outline


- Introduction
- Combinational logic
- Combinational circuits
- Sequential logic
- Structural modeling
- ***Testbenches***

Testbenches

- HDL code written to check if an HDL component works properly: the *device under test* (dut), or *unit under test* (uut)
- No synthesizable
- *Testbenches* types:
 - Simple
 - Self-checking

How to create a *testbench*

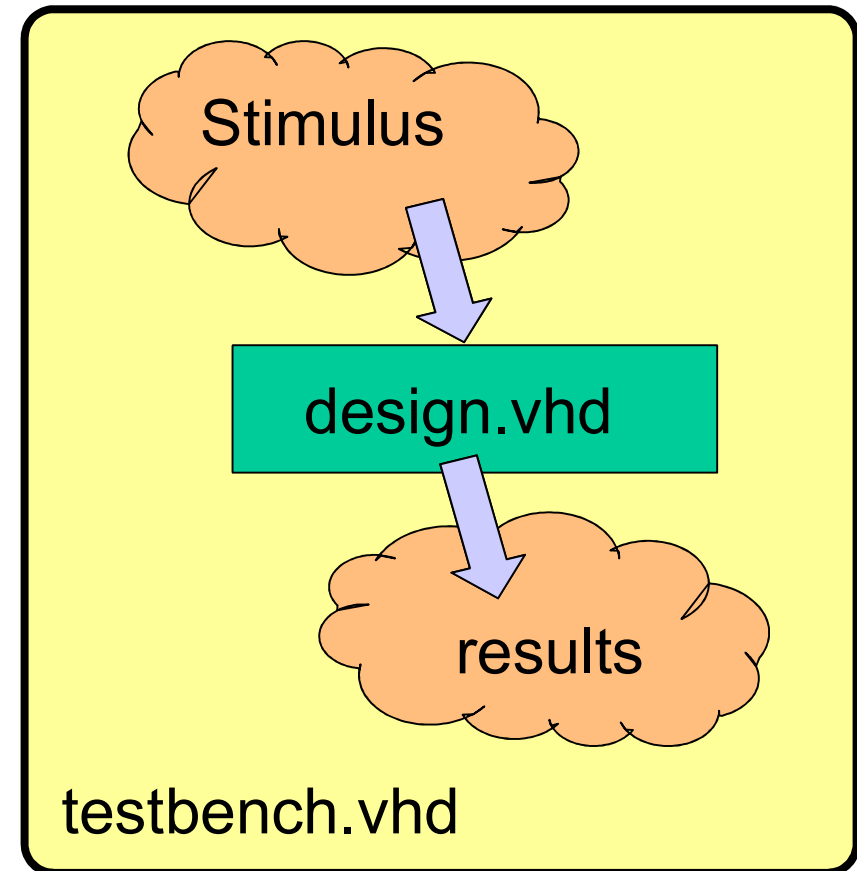1. Instantiate the design that we are going to verify
 - The *testbench* will be the new top-level component.
 - The entity won't have any ports
2. Write the code to:
 - Generate the stimulus
 - Check the results
 - Report the results to the user



Example

We are going to verify that this component works properly:

$$y = a \cdot b$$

VHDL

```
entity MyAnd is
    port (a, b : in std_logic;
          y : out std_logic);
end MyAnd;
```

```
architecture behavioral of MyAnd is
begin
    y <= a and b;
end behavioral;
```

Testbench (part 1, instantiation)

```
entity testbench1 is -- There are neither inputs
end;                  -- nor outputs (ports)

architecture test of testbench1 is
    component MyAnd      -- UUT declaration
    port (a, b: in std_logic;
          y: out std_logic);
    end component;
    -- Signals to connect the ports of the uut component
    signal a, b, y: std_logic;    -- Their names can be different
begin
    uut: MyAnd port map(
        a => a,
        b => b,
        y => y);
```


Testbench (part 2, gen. stimulus)

```
-- the stimulus are generated inside a process
process          -- There is no sensitivity list but there
begin           -- are wait sentences
    a <= '0'; b <= '0';
    wait for 10 ns;
    a <= '0'; b <= '1';
    wait for 10 ns;
    a <= '1'; b <= '0';
    wait for 10 ns;
    a <= '1'; b <= '1';
    wait for 10 ns;
    wait;        -- It "kills" this process. The process would
                  -- be restarted otherwise
end process;
end; -- end of the architecture
```

The simulation analyzes the value of 'y' signal in every case and check if it works properly

Self-checking

An *assert* sentence can be used to check the results

```
assert condition report "Message" severity level;
```

It verifies that `condition` is met. If not, it prints `Message` in the simulator Console and it generates an exception with the specified `level`.

Depending on the `level` (`note`, `warning`, `error`, `failure`), the simulator stops or not (it can be configured by the user).

MyAnd self-checking example

```
process -- There is no sensitivity list but there
begin    -- are wait sentences
    a <= '0'; b <= '0';
    wait for 10 ns;
    assert y = '0' report "Fails when 00" severity error;
    a <= '0'; b <= '1';
    wait for 10 ns;
    assert y = '0' report "Fails when 01" severity error;
    a <= '1'; b <= '0';
    wait for 10 ns;
    assert y = '0' report "Fails when 10" severity error;
    a <= '1'; b <= '1';
    wait for 10 ns;
    assert y = '1' report "Fails when 11" severity error;
    wait; -- It "kills" this process. The process would
    -- be restarted otherwise
end process;
```

Testbenches for sequential circuits

The clock is usually generated in a separate process:

```
process
begin
    Clk <= '0';
    wait for CYCLE/2; -- CYCLE is a constant
    Clk <= '1';
    wait for CYCLE/2;
end process; -- There is no wait, so the process
              -- will be restarted automatically
```

It is better to generate the clock only while one auxiliary signal is on, so the clock generation can stop when necessary. See the example of `while` loop.

Example of a counter

```
process -- There is no sensitivity list but there
begin   -- are wait sentences
    Reset <= '1'; -- the reset is always activated at the
                -- beginning
    wait for CYCLE;
    Reset <= '0'; -- It is deasserted so the counter starts
                -- to work
    for i in 0 to 255 loop
        assert to_integer(Count) = i
            report "Fails at " & to_string(i)
                severity error; -- Count is of type unsigned
        wait for CYCLE;         -- The clock is generated in parallel
                                -- with another process, see the
                                -- previous slide
    end loop;                  -- It finishes the loop
    wait;                      -- It "kills" this process
end process;
```

Sensitivity lists: *testbenches*

- The processes in *testbenches* can have no sensitivity lists
- In that case, it is necessary to write some *wait* sentence/s
- If there were no wait sentences, the simulator will get stuck, because the *time* wouldn't be able to advance (infinite loop)

Constants

- Like with any other language, you can use *constants* in VHDL.
- They are also declared in the declarative part, between *architecture* and *begin*, and the value must be provided in the declaration:

```
architecture example of test is
    constant C1 : std_logic_vector(3 downto 0) := "0101";
    constant C2 : integer := 5;
    constant CYCLE : time := 10 ns;
begin
```

- There is no restriction about the type of constant (std_logic, std_logic_vector, integer, time, etc).

Type conversion

- VHDL is *strongly typed* and there is no automatic cast:

```
architecture example of test is
    signal s1 : std_logic_vector(3 downto 0);
    signal s2 : integer;
    signal s3 : signed(3 downto 0);
    signal s4 : unsigned(3 downto 0);
begin
    s1 <= s2; -- Wrong in VHDL
    s2 <= s1; -- Also wrong
    s3 <= s1; -- Also wrong
    s4 <= s1; -- Also wrong
    s2 <= s3; -- Also wrong
    s2 <= s4; -- Also wrong
```


Type conversions

- Different functions are used for conversion in each case:

		TO			
		integer	signed	unsigned	std_logic_vector
FROM	integer		to_signed()	to_unsigned()	No direct conversion
	signed	to_integer()		unsigned()	std_logic_vector()
	unsigned	to_integer()	signed()		std_logic_vector()
	std_logic_vector	No direct conversion	signed()	unsigned()	

Unit 1: Digital design and VHDL

Escuela Politécnica Superior - UAM

Exercises U1

1.8.- Write the VHDL code of a multiplexer whose output is z, whose data inputs are a0, a1, a2 y a3, all of the type `std_logic_vector(31 downto 0)`. The control input is sel, of the type `std_logic_vector(1 downto 0)`. It is not necessary to include the entity or the architecture, only the behavioral part of the code (including process if necessary).

T

1.3.- “fuente” is `std_logic_vector(3 downto 0)` and “dest” is `std_logic_vector(6 downto 0)`. Write the code so that “dest” is equal to “fuente” multiplied by 8, but not using the any multiplication or addition.

1.9.- “dato4” is `std_logic_vector(3 downto 0)`. Write the VHDL code for getting that “salida8”, which is an `std_logic_vector(7 downto 0)`, is equal to dato4 but sign extended.

T

Exercises U1

1.2.- Write the equivalent code to the shown process, but using a concurrent assignment of the type when – else.

```
process(all)
begin
    if a < b then
        s <= b;
    elsif a < c then
        s <= c;
    else
        s <= a;
    end if;
end process;
```

1.10.- Write the equivalent code to the one given, but using a single case sentence. Add a process and its sensitivity list if necessary.

```
with s select
    z <= a when "00",
    b when "01",
    c when others;
```

1.16. Design a 4 to 1 multiplexer with 8 bits inputs using the following four sentences:

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;
entity Mux4a1 is
    port (
        D0, D1, D2, D3 : in unsigned(7 downto 0);
        Sel: in std_logic_vector(1 downto 0);
        Y: out unsigned(7 downto 0)
    );
end Mux4a1;
```

architecture ArchWhen of Mux4a1 is -- **a) Architecture based on sentence WHEN ELSE**

```
begin
    Y <=  D0 when Sel = "00" else
          D1 when Sel = "01" else
          D2 when Sel = "10" else
          D3;                             -- Sel="11"
```

architecture ArchIf of Mux4a1 is -- **b) Architecture based on sentence IF**

```
begin
    process (all)
    begin
        if Sel = "00" then Y <= D0;
        elsif Sel = "01" then Y <= D1;
        elsif Sel = "10" then Y <= D2;
        else Y <= D3;                     -- Used instead of Sel = "11" to avoid latches
        end if;
    end process;
end ArchIf;
```

1.16. Design a 4 to 1 multiplexer with 8 bits inputs using the following four sentences:

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;
entity Mux4a1 is
    port (
        D0, D1, D2, D3 : in unsigned(7 downto 0);
        Sel: in std_logic_vector(1 downto 0);
        Y: out unsigned(7 downto 0)
    );
end Mux4a1;
```

```
architecture ArchWith of Mux4a1 is    -- c) Architecture based on sentence WITH-SELECT

begin
    with Sel select
        Y <=
            D0 when "00",
            D1 when "01",
            D2 when "10",
            D3 when others;           -- "11"

end ArchWith;
```


```
architecture ArchCase of Mux4a1 is    -- d) Architecture based on sentence CASE

begin
    process (all)
    begin
        case Sel is
            when "00" => Y <= D0;
            when "01" => Y <= D1;
            when "10" => Y <= D2;
            when others => Y <= D3;    -- Closed with when others to avoid latches
        end case;
    end process;
end ArchCase;
```

Exercises U1

1.11.- clk, reset, d and q are std_logic signals. Write the code so that q is a D flip-flop active at falling edge and with asynchronous reset active at high level.

 1.14.- Write the VHDL code of the given circuit, which is a D flip-flop active at rising edge and with synchronous reset active at high level.



T

1.18. Write the code of an ascending 8 bits counters with asynchronous reset and parallel load.

T

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity Cont8Load is
  port (
    Clk , Reset, Load : in std_logic;
    Data : in unsigned(7 downto 0);
    Q : out unsigned(7 downto 0)
  );
end Cont8Load;
```

architecture Practica of Cont8Load is

```
begin
  PrCont: process(all)
  begin
    if Reset = '1' then
      Q <= (others => '0');
    elsif rising_edge(Clk) then
      if Load = '1' then
        Q <= Data;
      else
        Q <= Q + 1; -- normal behavior
      end if;
    end if;
  end process;
end Practica;
```


1.19. Write the code of an ascending 8 bits counters with asynchronous reset and parallel load whose data is chosen among 4 possibilities. Use the previous designed modules (multiplexer and counter).

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity Cont8Mux is
    port (
        Clk, Reset, Load : in std_logic;
        Sel : in std_logic_vector(1 downto 0);
        D0, D1, D2, D3 : in unsigned(7 downto 0);
        Q : out unsigned(7 downto 0)
    );
end Cont8Mux;
```

architecture Practica of Cont8Mux is

```
    component Mux4a1                      -- mux declaration
    port (
        Sel: in std_logic_vector(1 downto 0);
        D0, D1, D2, D3 : in unsigned(7 downto 0);
        Y : out unsigned(7 downto 0)
    );
end component;
```

```
    component Cont8Load                    -- counter declaration
    port (
        Clk, Reset, Load : in std_logic;
        Data : in unsigned(7 downto 0);
        Q : out unsigned(7 downto 0)
    );
end component;
```

```
    signal Data : unsigned(7 downto 0); -- It is only necessary to declare as internal signals those that go
                                         -- from one entity to the other, but are not ports (inputs or outputs)
```

1.19. Write the code of an ascending 8 bits counters with asynchronous reset and parallel load whose data is chosen among 4 possibilities. Use the previous designed modules (multiplexer and counter).

```
begin                                -- Instantiation and port mapping (by name)

    ElMux: Mux4a1 port map(          -- Instantiation of Mux4a1
        D0 => D0,
        D1 => D1,
        D2 => D2,
        D3 => D3,
        Sel => Sel,
        Y => Data
    );

    ElContador: Cont8Load port map(   -- Instantiation of Cont8Load
        Clk => Clk,
        Reset => Reset,
        Load => Load,
        Data => Data,
        Q => Q
    );

end Practica;
```

1.5.- Write an assert in order to test that the signal “s” is at ‘1’. If not, the simulation should output the text “Signal s is not at 1” and abort the simulation.

T

1.22.- Draw the schematic of the following VHDL code. All the connections must be labeled in the schematic. A is std_logic_vector(7 downto 0). All the components must be correctly identified with their standard symbol or an explanation of the functionality in text.

```
process(all)
begin
    if rising_edge(Clk) then
        if CE = '1' then
            if X = '1' then
                Y <= resize(A,16);
            else
                Y <= A & "00000000";
            end if;
        end if;
    end if;
end process;
```

1.17.- Design a testbench for the 4 to 1 multiplexer of the exercise 1.16.

1.17. Design a testbench for the 4 to 1 multiplexer of the exercise 1.18:

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;
```

```
entity Mux4a1Tb is
end Mux4a1Tb;
```

```
architecture Test of Mux4a1Tb is
```

```
entity Mux4a1 is
  port ( D0, D1, D2, D3 : in unsigned(7 downto 0);
        Sel: in std_logic_vector(1 downto 0);
        Y: out unsigned(7 downto 0) );
end Mux4a1;
```

```
  component Mux4a1
    port ( D0, D1, D2, D3 : in unsigned(7 downto 0);
          Sel: in std_logic_vector(1 downto 0);
          Y: out unsigned(7 downto 0) );
  end component;
```

-- Declaring the entity to be tested

```
-- One signal for each port of the previous component. The names could be the
-- same as in the Mux4a1 entity, but different names can also be used.
```

```
  signal sD0, sD1, sD2, sD3, sY : unsigned(7 downto 0);
  signal sSel : std_logic_vector(1 downto 0);
```

```
  constant CICLO : time := 10 ns;      -- Time constant
```

```
begin
```

```
  uut: Mux4a1 port map (                -- Instantiation of the tested circuit (Unit Under Test)
    D0 => sD0,
    D1 => sD1,
    D2 => sD2,
    D3 => sD3,
    Sel => sSel,
    Y => sY
  );
```

1.17. Design a testbench for the 4 to 1 multiplexer of the exercise 1.18:

T

```
ProcPrinc: process          -- Continuation of the architecture
begin                      -- Generate values for the inputs and check the outputs
    sD0 <= (others => '0');
    sD1 <= "00000001";
    sD2 <= X"02";
    sD3 <= (1 downto 0 => '1', others => '0');

    sSel <= "00";
    wait for CICLO;
    assert sY = sD0 report "Error in the 00 selection" severity failure;

    -- A signal that is not updated keeps its previous value.
    sSel <= "01";
    wait for CICLO;
    assert sY = sD1 report "Error in the 01 selection" severity failure;

    sSel <= "10";
    wait for CICLO;
    assert sY = sD2 report "Error in the 10 selection " severity failure;

    sSel <= "11";
    wait for CICLO;
    assert sY = sD3 report "Error in the 11 selection " severity failure;

    report "Always enters as false is not true" severity note;
    wait;          -- Kills the process. As this is the only process, the simulation ends here
end process;

end Test;
```